

Voltage stabilizer and UPS

Objectives: At the end of this lesson you shall be able to

- state the basic concept of stabilizer
- draw the block diagram and explain the function of each blocks
- state the working various types of voltage stabilizers
- state the basics of UPS system
- explain the block diagram of OFF line UPS and its various controls and functions
- explain the block diagram ON line UPS and advantages and disadvantages.

Voltage stabilizer

It is an electrical supply device controlled by electronic circuit which gives the constant output voltage irrespective of the variation in the high input supply voltage or disconnect the output circuit if the input voltage is very low or very high.

Every electrical device is designed to operate at a certain rated voltage for optimum efficiency and maximum length of service. Power supply voltages should not drop or rise by more than 5% of rated voltage as per IS.

The effect of voltage variations in commonly used electrical appliances are given below.

Sl.No.	Name of the equipment	Low voltage	High voltage
1	Incandescent lamp	Lamp efficiency decreases if the voltage is decreased.	Life of the lamp decreases or the lamp fuses in extreme cases.
2	Fluorescent lamp	If voltage is too low, lamp will not light up.	Life of the tube/choke decreases.
3	Electric stove, electric iron, water heaters, toasters etc.	Increases the heating time as heat produced is low.	Shortens the life of heating elements or heating elements burnt out.
4	Fans, vacuum cleaners	Efficiency decreases.	Life of the equipment is decreased
5	Washing machines, refrigerators and air-conditioners	Motor of the machine will draw more current from the line that results in overheating of the motor which may lead to burn out.	The motor insulation may fail and draw excess current which can lead to burn out.
6	Radios and television sets	Poor quality of reception, picture will not be clear in the television sets.	Life of the equipment is decreased

Some of the electronic equipment such as colour television sets are designed by the manufacturers with built in electronic stabilizers like Switch Mode Power Supplies (SMPS). Hence there is no need to provide an additional external stabilizers for these equipments.


Types of AC voltage stabilizers


- 1 Stepped voltage stabilizer
 - a) Manual
 - b) Automatic relay type
- 2 Servo voltage stabilizer
- 3 Constant voltage transformer

Stepped voltage stabilizer

In the stepped voltage stabilizer, an auto-transformer is used for regulating the output voltage. A manually operated

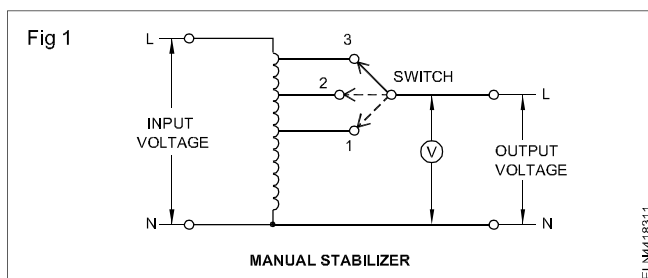switch as in Fig 1 regulates the output voltage in the manual type. In automatic relay type stabilizers a sensing circuit actuates the relays which regulates the output voltage. The schematic diagram in Fig 2 is for an automatic relay type stabilizer.



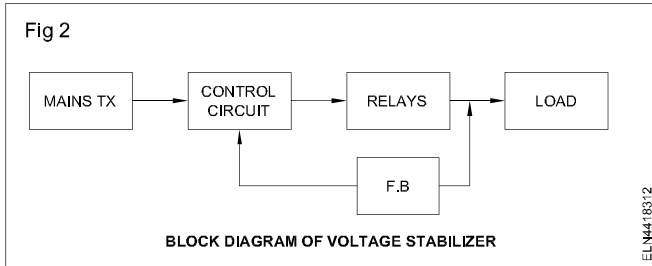

Mains Tx


This transformer supplies two level voltage i.e, low voltage and high voltage, which is to be supplied according to the needs. Some stabiliser working in buck boost operation to meet special application for load requirements. The auxiliary supply also provides for control circuit requirements by the mains transformer.

Control circuit

In the ordinary voltage stabilisers, control circuit regulate the relay operation, irrespect or output voltage. When input voltage falls below the set voltage H. T side relay will operate and incase high voltage condition LT side relay will operate and maintain the stipulated operate voltages. The relay operation controls by controlling relay coil supply which is set for separate DC regulated voltage levels.

Relays

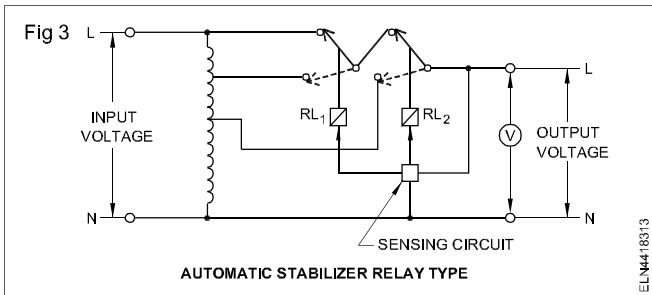It is a electromagnetic relay which operates two different coil voltage. the DC coil voltage decides which relay has to be operate depends on the input AC voltage supplied to the transformer. Fig 3 shows an automatic relay type stabilizer.




Feed back

In non automatic voltage stabiliser DC voltage are taken on the feed back quantity, which operates the relay coil. The coil DC voltage will be two different voltage to activate the relay in case of low and high voltage AC input conditions.


Load

Load can be anything connected to the stabiliser. Some electrical equipments requires a constant input voltage to operate. such case a stabiliser is required. But in automatic stabiliser have the disadvantage of transient line (Change over to one voltage to other voltage level) which may cause the stabiliser to OFF condition few milli seconds.

Stepped voltage stabilizer - manual type : Fig 4 shows an auto-transformer in which the output voltage increases as the tap changing switch S_1 is turned clockwise. The output voltage can be seen by connecting a voltmeter in the output side as in Fig 4. Increasing or decreasing the output voltage near to the set value is possible by rotating the tap changing switch S_2 in the appropriate direction within $\pm 10\%$ of the desired output voltage. A push-button switch S_1 enables to measure the incoming voltage.

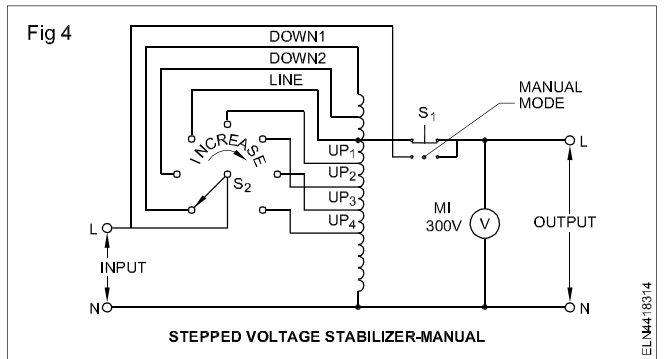

Stepped voltage stabilizer - automatic type : Fig 5 shows a stepped voltage stabilizer of the automatic type operated by relays. T_1 is an auto-transformer with multiple tappings. S_1 and S_2 are two secondaries for relay operation. The secondary voltage of S_1 is rectified and filtered for the use of the sensing circuit while voltage S_2 is rectified and filtered for the use of the relay operation. P_1 and P_2 are pre-set resistors (variable resistors) used for adjustment. R_1 , P_1 and R_2 provide sensing voltage to the zener diode. DZ_1 and R_3 , P_2 and R_4 to the zener diode DZ_2 . Q_1 and Q_2 are two transistors used as switches. RL_1 and RL_2 are two relays.

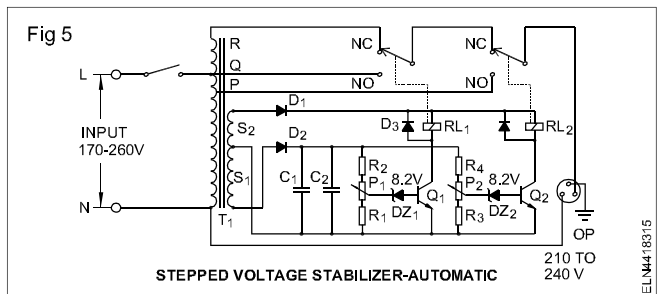

When the input voltage is low, say less than 200V, both DZ_1 and DZ_2 do not conduct as the voltages at the preset tappings are less than their zener diode voltages. This causes both transistors to cut off and the relays are in the off position. At the off position of the relays, NO contacts of both the relays connect terminal R of the auto-transformer to output which results in booster output voltage.

When the input voltage increases above 210V, but below 240V voltage across S_1 increases proportionally. This increases the pre-set tap voltage, thereby the zener diode DZ_1 conducts and hence make the transistor Q_1 to ON. The relay RL_1 operates and connects the supply voltage directly to the output through NO. contact of RL_1 and NC contact of RL_2 . By this operation the output voltage will be the same as the input voltage.

When the input supply voltage increases above 240V the zener diode DZ_2 gets voltage from P_2 and hence conducts which makes Q_2 to ON. This results relay RL_2 energise and output is taken from NO. point of RL_2 . The output voltage reduces or bucks.

Usually 12V DC relays with the required current ratings of contacts are preferred for stabilizers. Diodes or capacitors are used across the relay coil to protect the transistors from reversed induced emf when the relays become OFF. LED indicators are sometimes used to indicate the mode of operation such as buck, normal, boost etc.

Stepped voltage stabilizers are available with different types of electronic circuits with one to three relays to provide an output voltage of 200-240V. They are specified for maximum input voltage variation and for their output, KVA ratings say 170 to 270 volts 1 KVA or 135 to 260 volts 0.5 KVA.


Some of the stabilizers are provided with over-voltage and under-voltage cut off to protect the connected equipment.

Applications : Stepped voltage stabilizers are used along with refrigerators, air conditioners, TVs, VCRs etc. Colour TVs with self-contained switch mode power supplies do not require voltage stabilizer as they are designed to operate from 130 to 260 volts.

Servo - voltage stabilizer

The servo voltage stabilizer employs a toroidal auto-transformer and a servo motor driven by a sensing circuit which senses the voltage. The difference between the output and nominal voltage is sensed by a sensing circuit which drives the servo motor. Any variations in mains cause the motor to move clockwise or anticlockwise thus correcting the voltage.

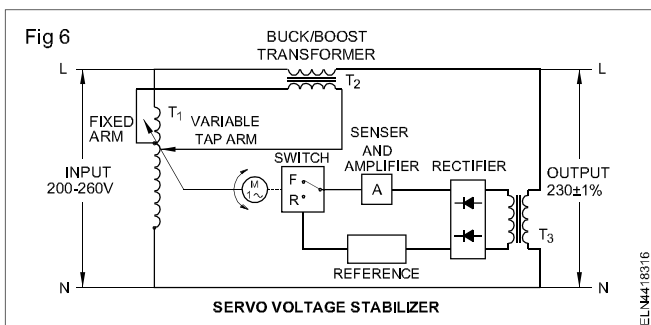A servo voltage stabilizer is provided with three transformers function along with control circuits and a servo motor as in Fig 6. T_1 is a continuously variable toroidal auto-transformer (variac) driven by a servo motor M.



The output from the variac, drives a series buck/boost transformer T_2 so that boost takes place when the variable tap arm moves down and bucks the voltage when the arm moves up. The transformer T_3 provides the required reference voltage and sensing voltage for the electronic circuit which drives the motor.

When the output voltage is less than the reference voltage, the electronic circuit senses the difference, drives the motor in one direction which results in increase in the output voltage.

When the output voltage increases above the ratings, the motor is driven in the opposite direction so that the output voltage increases. When the voltage difference in output and the reference are equal, the servo motor is switched off by the circuit.


A servo stabilizer provides constant voltage to an accuracy around $\pm 1\%$ or $\pm 0.5\%$ and a correction range 10 to 30 volt/sec.

A servo stabilizer is more accurate and also costlier, and, therefore, used with costlier equipments such as computers, xerox machines, medical electrical equipments etc.

Constant voltage transformer

A constant voltage transformer works on ferro-resonant principle. The variation in the primary flux with an unsaturated iron core does not affect the secondary flux with saturated iron core. Thus, the secondary induced voltage remains relatively independent of the voltage impressed upon the primary winding.

In an ordinary transformer, the primary and secondary coils are closely coupled. Any change in primary voltage is directly transferred to the secondary in the ratio of the number of turns. In a CVT, the primary and secondary coils are loosely coupled. These are wound on separate sections of the transformer core as in Fig 7. In between the coils, a separate shunt path is provided for the flux to flow but an air gap is provided in the shunt path. A capacitor is provided in parallel with the secondary.

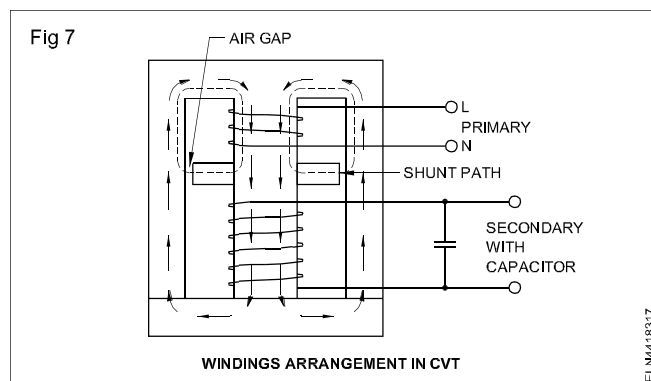


Now imagine what will happen when voltage is applied to the primary. Starting from zero, if the voltage increases slowly, initially, all the flux generated by the primary voltage will pass through the lower half of the transformer core because the air gap in the shunt path will prevent it from taking this path. This is shown by bold arrows in Fig 6. As a result, the rise in secondary voltage is proportional to the primary. But as voltage in the secondary coil rises, at a certain point the impedance of the coil will become equal to the impedance of the capacitor, i.e.

$$X_L = X_C \text{ or } 2\pi fL = \frac{1}{2\pi fC}$$


This is the condition of resonance, and at this point a high current will flow in the LC circuit. This high current will result in a sudden rise of voltage across the secondary (Fig 6), and the core in this section of the transformer will saturate.

Once the core gets saturated, it prevents the entry of further flux coming from the primary side. Therefore, any increase in flux due to increase in primary voltage has to take an alternate shunt path as in Fig 7. Hence, very little increase in the secondary voltage takes place. This little increase can also be nullified by a feedback-FB winding connected as in Fig 8. The output winding can be separated from the capacitor circuit if the voltage required is low or tapings can be taken out of the capacitor.

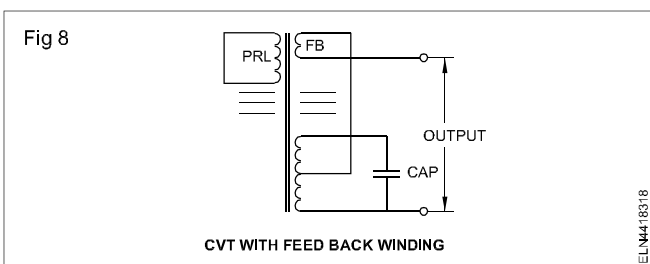

CVT may not be suitable for an instrument in which SCR power supply is used or an inductor or a capacitor is coming in the AC circuit or a motor drawing a heavy in-rush current is used inside the instrument. But it is suitable for electronic machines such as TVs, computers, FAX machines etc.

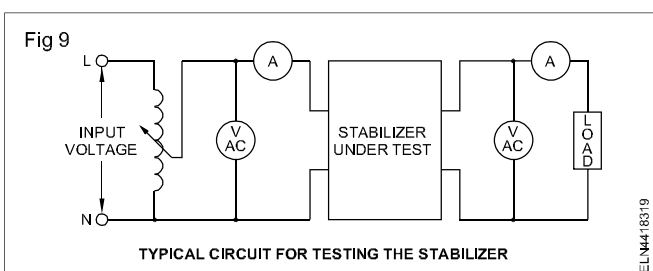Testing a stabilizer : To test a stabilizer for its operating range, a variac and rated load along with voltmeters/ammeters are necessary. A simplified circuit for testing the stabilizer is given in Fig 9.



By connecting the stabilizer as shown in the figure above and varying the input voltage to the range specified in the name-plate detail such as 170 to 260V or 130 to 270V etc. The output voltage should be satisfied with the specified voltage such as 200 to 240V. There should not be any undue heating or failures with the rated load for a continuous working.

Basics of UPS systems

Most people take the mains AC supply for granted and use it almost casually without giving the slightest thought to its

inherent defects and the danger posed to sophisticated and sensitive electronic instruments. For ordinary household appliances such as incandescent lamps, tubes, fans, TV and fridge, the mains AC supply does not make much of a difference, but when used for computers, medical equipments and telecommunication systems, a clean, stable, interruption-free power supply is of utmost importance.

As more and more personal computers, word processors and data terminals find their way into small business, UPS systems that meet the power requirements and price range needs for small business and offices are being manufactured.

The ever increasing importance of computers in industry and commerce will increase the need for quality, high stability and interruption-free power supplies.

Earlier Data Operating System (DOS) does not have any shut-down procedure. So in case power failure it does not affect the operating system. Latest operating system Windows 9x and application softwares require proper shutting down and exit procedures. This procedure requires time which is provided by UPS in case of mains power failure.

UPS (Uninterrupted Power Supply) is the only solution available to an individual customer faced with the problem of ensuring high quality of power for critical loads. All UPS designs contain a battery charger to keep the battery fully charged by the power from mains. Small UPS normally comes with a sealed maintenance free (SMF) batteries which can provide 10 to 15 minutes of power backup, the backup time increases with the capacity of the battery. Tubular batteries or automotive batteries are used in medium and large capacity UPSs.

UPS classification

There are two broad categories of UPS topologies - OFF line, and ON line. These topologies differ in the way they serve the load when the mains is present and is healthy. They vary in features & pricing.

OFF-Line and ON-Line

OFF-Line UPS filters the mains and feeds it directly to the load for most of the time. When the mains is unhealthy, perhaps due to a slight drop in voltage, the load is switched by a fast relay, in typically less than half a cycle, to an inverter deriving its power from a battery. The inverter generates a square or stepped waveform to emulate the mains-satisfactorily for most computers. This particular technique represents the lowest cost solution.

Online UPS converts AC mains into DC before inverting again to AC to power the load with a synthetic sine wave. A battery connected across the DC link acts as the backup power source.

This gives a supply for the computer that totally isolates the input mains from the load, removing all mains noise and with no break when the mains fails.


Standby/OFF Line block diagram (Fig 10)

In the off line UPS, the load is connected directly to the mains when the mains supply is available. When working over voltage/under voltage conditions are detected on the mains, the off line UPS transfers the load to the inverter. When the line is present, the battery charger charges the battery and the inverter may either be shut down or will be idling. Thus in an off line UPS, there is a load transfer involved every time, the mains is interrupted and restored. This transfer is effected by change-over relays or static transfer switches. In any case there will be a brief period during which the load is not provided with voltage. If the load is a computer and the transfer time is more than 5ms, then there is a chance that the computer will reboot.

Some modified designs incorporate a limited range of voltage regulation by transformer tapping and a certain degree of transient protection by using RF filters and MOV's (Metal Oxide Varistor). Offline UPS is an economical and simple design and hence it is preferred for small rating, low cost units aimed at individual PC user's market. When the load is really a critical one an off line UPS is not acceptable. Usually square wave output off line UPS are available in market with lower loading capacities.

Advantages of OFF line UPS: High efficiency, small size, low cost.

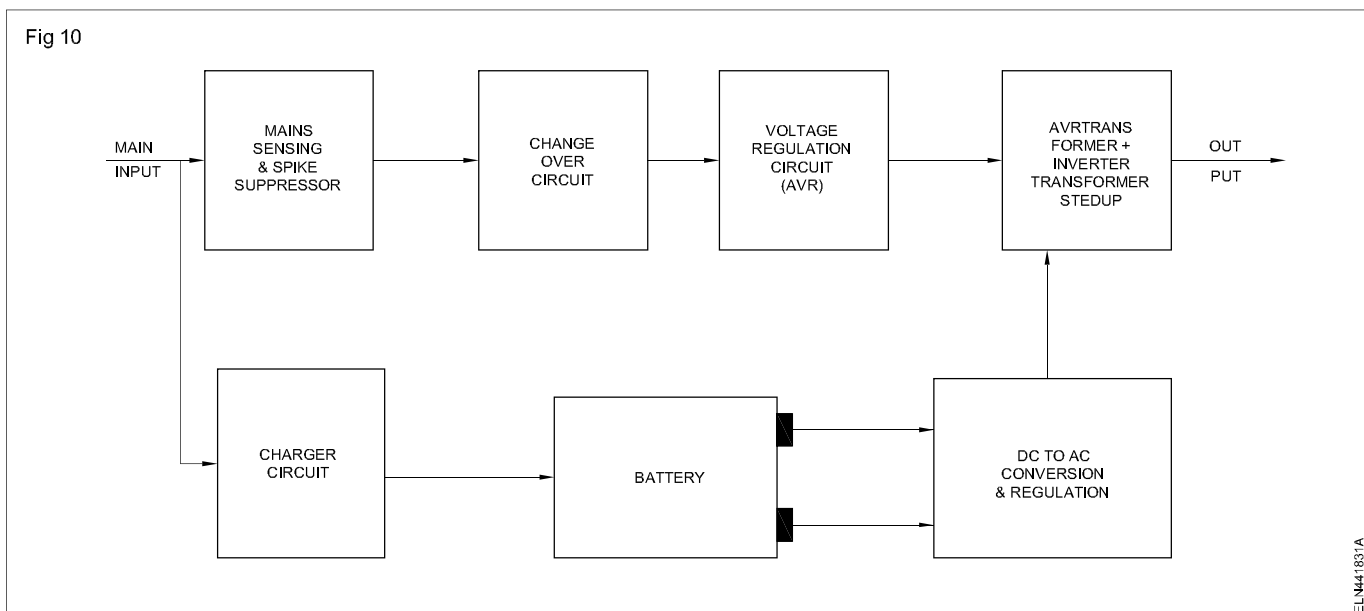Disadvantages: There can be change over complaint in offline UPS. Off line very much depends on battery. If battery fails entire system fails. Sometimes during change-over computer re-boots which causes loss of files. Another disadvantage is that output voltage will be a varying one. Usually in the range of 200V-240V and hence not suitable to all electronic gadgets.



Front panel indications and rear panel sockets/ switches used in UPS

All UPS systems have

- Fuse/Fuse holder
- Switches
- Sockets
- Panel indicator (LED and Neon lamp)
- Meters (Volt/Ampere)

Fig 11 and 12 shows the front and rear panel controls/ sockets.

Switches: On/Off switch and reset switch are commonly used in UPS. Reset switch is used to cut off an overload circuit and restart the supply. This is a push to off switch. In normal position this switch keeps the circuit on and when pushed, it cuts off the circuit.


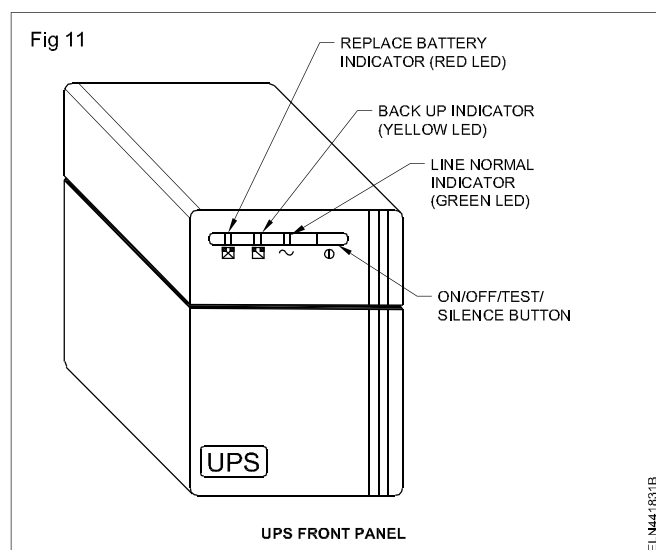


Fig 12

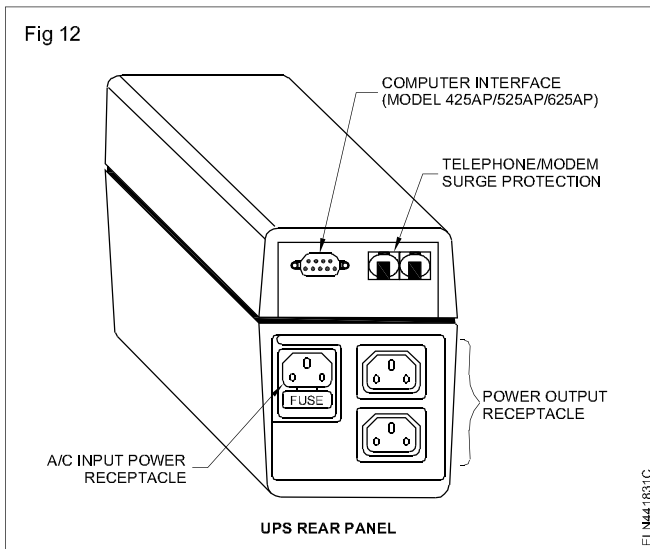

Socket: A common 5 Amp. or 15 Amps. three pin power output socket is used in UPS to provide UPS output to the various devices. One can connect an ordinary 5/15Amp. plug to the UPS output.

Different LED indications/buzzers that are used in UPS

Mains ON indication: It indicates mains input is present and UPS is working on mains.

Mains Low indication: It indicates that mains input is low and is below a rated value.

Mains high indication: It indicates mains input is high.

Inverter ON indication: It indicates that UPS is working in the battery mode and mains is absent.

To get the output from UPS switch ON the 'Inverter ON' switch.

UPS Trip indication: It indicates that UPS output is Off or tripped.

Overload indication: Which indicates that the load current is above a pre-determined value.

Overload buzzer: It beeps whenever overload occurs.

Low battery warning: It indicates battery voltage is below a pre-determined value along with a buzzer.

Battery charging indication: It indicates that battery is charging properly.

Output voltage low indication: It indicates that output voltage is below a pre-determined value.

General specifications & UPS protections

UPS are available from 500VA to 20KVA or above. VA is voltampere.

Power factor specification will be different for different manufactures. Suppose for 1 KVA UPS with a power factor 0.6 the load will be $1000 \times 0.6 = 600$ watts.

Normally a single PC takes around 180 watts. There are sine wave, square wave and quasi square wave output UPS. Usually sine wave out UPS is better than square wave output UPS.

General specifications

Output capacity = Output capacity will be in volt amperes (VA)

Input voltage = 230V AC $\pm 20\%$, 50 Hz single phase sine wave

Output voltage = 230V AC $\pm 10\%$, 50 Hz square wave or sine wave

= 230V AC $\pm 2\%$, 50 Hz (for ON-Line)

Battery = 7 AH, 12V Sealed Maintenance Free (SMF) for OFF-Line (depends on the capacity of the UPS)

= Tubular batteries from 40 AH to 160 AH (12V to 120V) for ON-Line (depends on the capacity of the UPS).

Availability of Automatic Voltage Regulation (AVR) feature.

Typical recharge time to charge 90% of the full capacity of the battery is 5 hours.

Different types of protection in UPS

Input fuse on mains: It protects the system from high voltage inputs, line disturbances and short circuiting etc.

MOV (Metal Oxide varistor) protection: MOV conducts when high input voltage appears thereby blowing the fuse

Polyester capacitor for lightning protection: This is connected across the transformer winding. It burns when lightning occurs and protects the transformer.

Fuses to protect the MOSFETS: MOSFETS are highly sensitive to rapid changing currents. These fuses are used to protect the MOSFET.

Charger fuse to protect the charger circuit: If any fault in charger circuit occurs, fuse blows to protect SCRs.

Output high voltage protection MOV: This MOV is connected across output sockets phase and neutral. If feedback circuit fails the output voltage will jump to more than 300 volts. In such situation the MOV conducts to protect the load.

Overload protection: It protects the UPS especially MOSFET/IGBT when output current exceeds a preset value (overloading the UPS). When this occurs, UPS output becomes OFF along with an indication.

Battery over charge/discharge protection: It protects the battery from charging to a high value (SMF batteries will charge upto 15.8V) and tubular batteries upto 14.1V. It also protects the battery from getting discharged below a level (low battery protection). If the battery voltage is discharged below 10.5V, then the UPS gets automatically switched OFF.

General tips for testing a UPS

- Connect the battery to the terminals using a fuse wire. If any fault occurs in testing the fuse will blow to protect the UPS.
- Do the testings on no load condition.
- Check the gate voltages of the two MOSFET banks it should be the same. If PWM gate pulses are not present gate voltage will be around 5.6V. If the PWM gate pulses are present then the gate voltage will be around 2-2.5 volts.
- Some frequency meters are designed to measure pure AC frequency only. If the UPS output is square wave, then the reading will not be correct. To measure the correct frequency connect a 60/100W load at the output of the UPS. Then the frequency meter shows a near correct frequency.
- For overload setting in ON-Line UPS, the load current is calculated by dividing the maximum load with the output voltage. This can also be measured using a clamp meter on the output terminal. Overload is set at this value of load current.
- While using extension boxes either in the input or on the output of an UPS, ensure proper earth connection. Improper earthing may lead to poor line filtering and shock hazards.
- If number of MOSFETs are connected in parallel, care should be taken to see that all the MOSFETs are of the same Rds. For MOSFET Rds value (drain to source resistance) and current rating are important.

Changeover in OFF-Line UPS system

In this type of UPS, the relay controls the battery voltage which is applied for relay coils. If the battery voltage is too low then relay coil will not get sufficient supply to trigger the switch. This may lead to the absence of mains voltage, even if mains is present and is healthy. This type of OFF-Line systems are battery dependent.

Some OFF-Line systems are battery independent. The coil supply is provided by the mains itself. Mains supply is reduced and rectified. This rectified supply is given to the changeover relay coil. Battery low voltage does not affect the relay coil supply. This type of OFF-Line UPS provides mains output irrespective of the battery condition.

Isolation of inverter

Another important point is that the isolation of the inverter section during the presence of mains, this is done by the change over relay. For inverter side isolation a switching transistor is used. This switching transistor controls the shut down pin voltage of oscillator IC. This transistor makes this pin high when mains is present.

Once shut down pin becomes high, oscillator IC stops generating pulses to MOSFETs. MOSFET becomes OFF and inverter section becomes inactive. When mains failure occurs this pin voltage is changed by the transistor to generate gate pulses.

The inverter section of OFF-Line and ON-Line UPS are almost same except in the mains section.


OFF-Line UPS employs a mains delay capacitor. This is a prevention to fast varying mains input voltage. If mains condition is changing rapidly (Mains ON/OFF) then the UPS has to switch alternately to battery mode and mains mode. Since MOSFET cannot respond to these fast varying currents it will burn. To avoid this, a delay capacitor in mains mode (.1Mf) to delay the mains input. As soon as mains is sensed by the opto coupler, mains on indication glows. Changeover relay will respond after a few seconds to mains because of this capacitor. Removing this capacitor decreases changeover time. But this may cause damage of MOSFET.

ON line UPS

In an ON line UPS, the inverter always supplies the load irrespective of whether mains power is available or not. The load is always left connected to inverter and hence there is no transfer process involved. When the mains power is present, it is rectified and applied in parallel with the battery. Hence all the supply system transients are isolated at the battery and the inverter always delivers pure sine wave of constant amplitude to the load.

Fig 13 represents a basic block diagram of an ON Line UPS.

In the block diagram (Fig 13), the mains input is stepped down to a lower level and applied to a thyristor based phase controlled AC to DC converter, employing firing angle(α) control. The PWM inverter which usually employs pulse width modulation using triangular/square wave carrier runs in battery mode. The output is filtered and given to the load. The PWM inverter is switched in the frequency range (50Hz) depending on the power rating and hence the DC side current drawn by the inverter will contain switching frequency components.

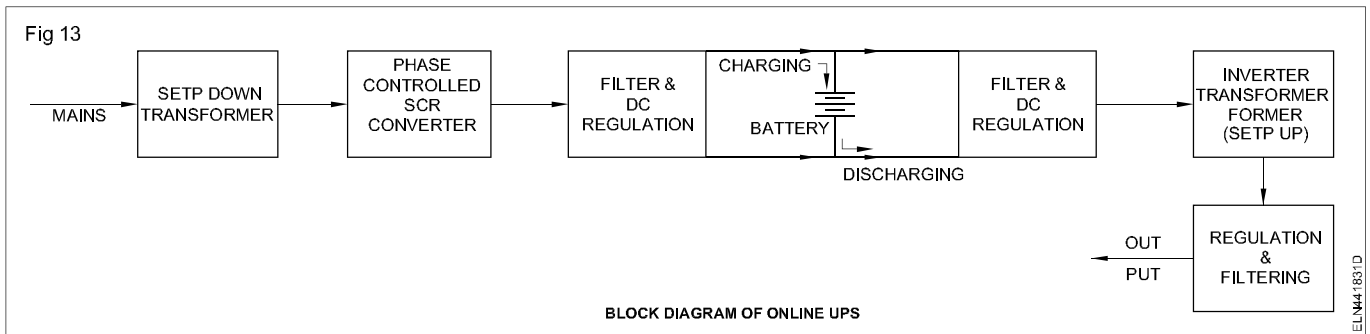

Along with the charging current the second harmonic component of DC side current of the inverter also flows into the battery. This second harmonic is quite large in value and this represents unnecessary strain on the battery. This is one of the major disadvantages of this design since it affects the battery life adversely.

When the mains is present the load power flows through the converter, reaches the battery node and from there flows into the inverter i.e there is double conversion of power. The converter, Inverter and the two level shifting transformers incur power losses in this process. Hence the efficiency of this design is lower than the OFF line design.

In a properly designed control system the battery voltage is measured and compared with a set float voltage. The error is processed in a proportional controller and the processed error decides the charging current that should flow into the battery. Charging current will be a constant one for ON line UPS.

Often it is found that the battery is in discharge mode even when mains is present i.e the battery shares the load current with the mains. This happens when the mains voltage is low and/or the output is loaded to above 75%. The efficiency of ON line UPS can be increased by using boost type power factor correction circuit.

Advantages

- Constant output voltage (No AVR card) free from changeover problem.
- Constant charging current.

Disadvantages

- complex in design, lower efficiency, higher cost, bigger in size and strain on the battery.

Presets of an ON-Line UPS

The presets of ON Line UPS are different from the OFF Line.

ON-Line UPS presets

Output high cut preset: Suppose there occurs a failure in PWM or feedback section. The output voltage will jump above 300V AC. This much output voltage causes harm to the output load. To prevent this output high cut preset is used. When the output voltage reaches set limit, this preset cuts the output. To set this limit, increase the output voltage using the PWM output voltage control preset till it reaches 265V and set the output high cut preset to shut off the output.

Emergency light

Objectives: At the end of this lesson you shall be able to


- explain the block diagram of emergency light
- explain the emergency light circuit diagram and charging of battery.

Emergency light

Emergency lighting system is commonly used in public building, work places, residences etc., The main function of the emergency lamp in the industry are


- to indicate ESCAPE routes
- to provide illumination to path ways and exit
- indicate the location of the fire fighting equipments.

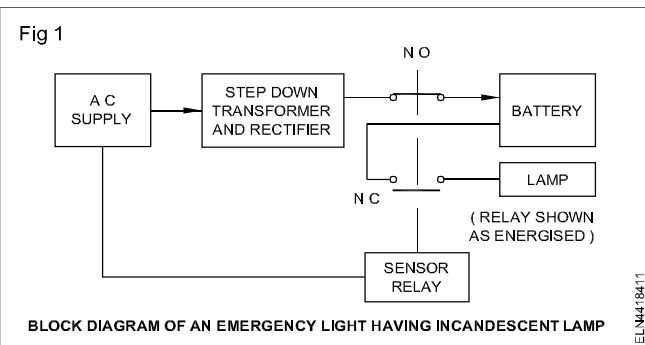The block diagram of an emergency light is in Fig 1. The circuit is discussed here are basic circuits without over charging protection for battery or trickle charging facility. Modern emergency lights have these facilities.



As shown in the block diagram AC main supply is fed to the step down transformer, then it is rectified to charge the battery through a sensor relay. A lamp is connected in the battery circuit through the relay. When AC supply fails the relay enables the battery to the connected lamp circuit through the normally closed contact and the lamp will glow.

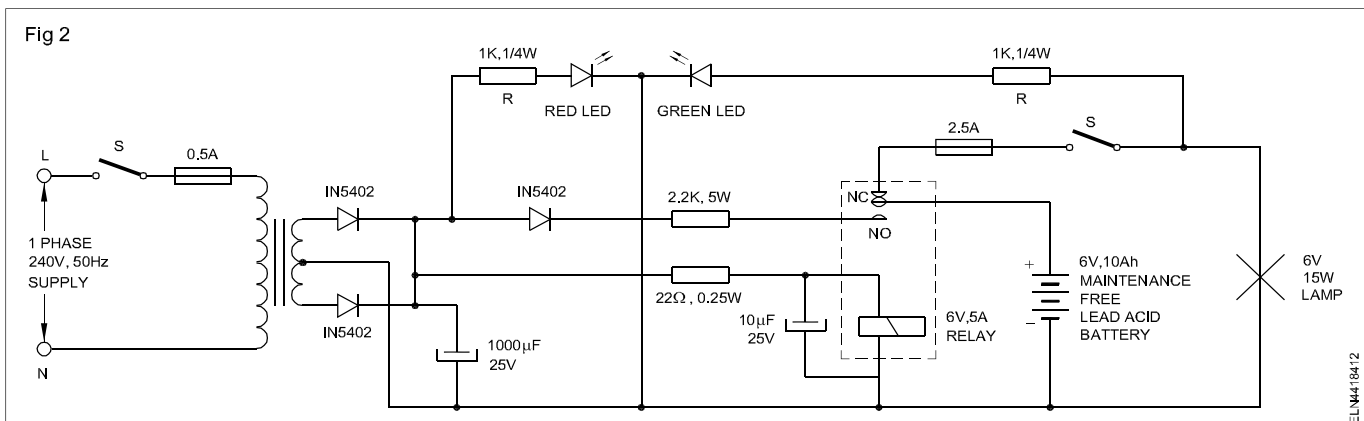When the AC supply is restored, the battery will be getting charged through the normally open contact of the relay. The charging current is regulated by the series resistances of 2.2 ohm, 5 watt. as in Fig 2. The two LEDs, one is red



and the other is green are provided in the circuit to indicate the presence of AC and the lighting of the lamp through the battery supply respectively.

One 1000 microfarad capacitor is used in the rectifier circuit to smoothen the output D.C. supply and one 10 microfarad capacitor is used across the relay to increase the efficiency of relay operation.

Emergency tube light circuit: The emergency light which is connected to an ordinary incandescent lamp will give less light. If the fluorescent tube is used in emergency light it will give about 3 times more light consuming same wattage. Hence most of the emergency lights are incorporated with fluorescent tube lights.

The inverter circuit is incorporated with the ordinary incandescent lamp could be replaced by a tube light as shown in the block diagram, (Fig 3). The tube light requires a high voltage for its operation. The inverter is used to convert DC supply to AC and then it is stepped up to light the fluorescent tube. The inverter circuit is made operative by the sensor (relay). When AC supply is not available, during power failure battery voltage operates the inverter, in which DC is converted to AC and then stepped up to high voltage to enable the fluorescent tube to light up.


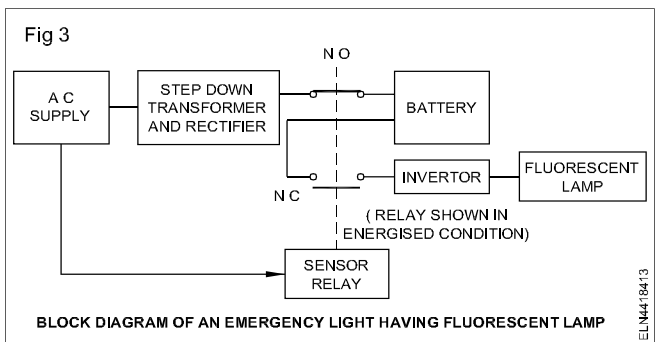


Fig 4

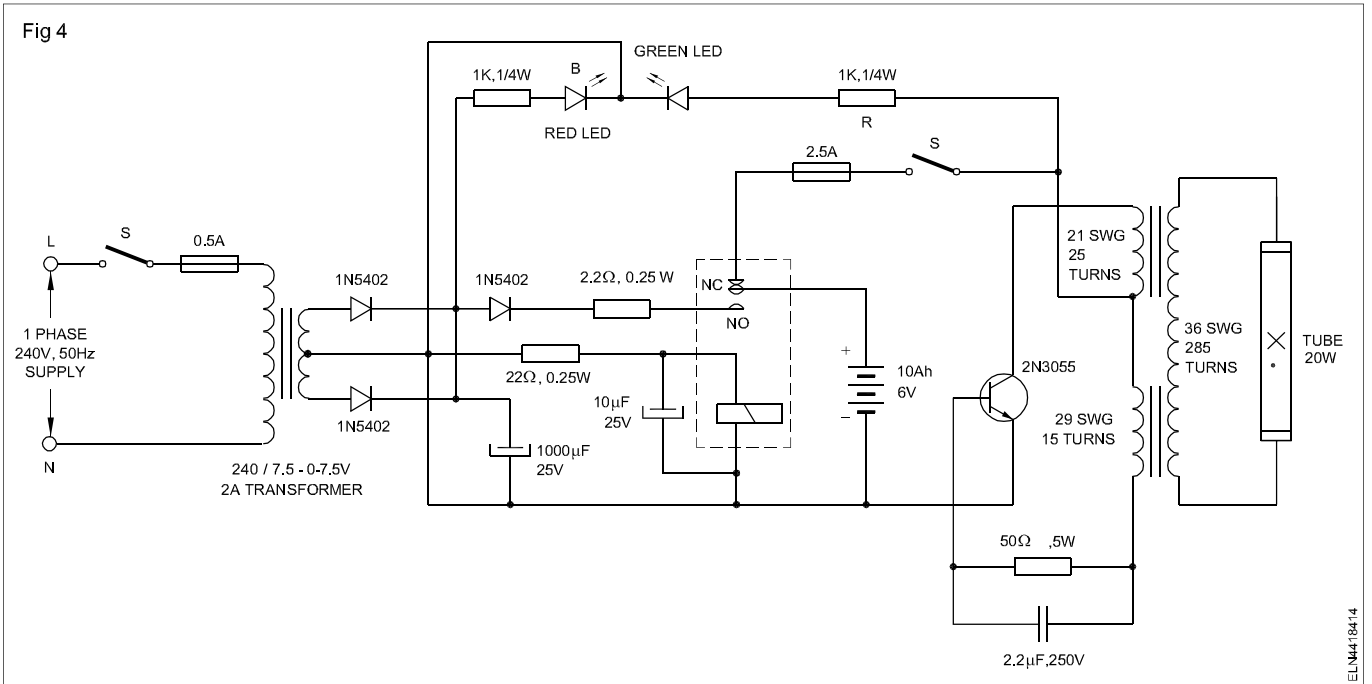

ELN4418414

Inverters are basically transistorised oscillators as in Fig 4. They can be made to oscillate at the frequency of about 6.6 kHz. The frequency of the circuit can be changed by changing the value of resistor and capacitor in the circuit which is connected in the base of the transistor.

When the AC supply is resumed the sensor relay connects the battery terminals to the rectified DC circuit for charging

and the inverter circuit is disconnected from the circuit by the relay.

For keeping the temperature of the power transistor within its temperature range suitable heat sink should be mounted over the power transistor.

Battery charger and inverter

Objectives: At the end of this lesson you shall be able to

- explain the working of battery charger with the help of block diagram
 - describe various batteries and its maintenance, rating, methods of charging
 - explain the battery charging circuit and its auto-cut-off
 - state the principle of inverter with the help of block diagram
 - explain power inverter and input output voltage, frequency, power relations.
-

Battery charger

Proper selection and maintenance of the battery is very essential for the proper working of battery wherever is used: such as inverter, UPS etc

Many types of battery used for different purpose. Each have more advantages and disadvantages.

Commonly the following four types of batteries are used with the inverter systems, UPS etc.

- Automobile batteries
- Tubular/Industrial lead acid batteries
- Sealed maintenance free (SMF) batteries
- Nickel cadmium batteries

Automobile batteries

This type of batteries are commonly used in automobile, cars, trucks etc. It is cheapest of the other batteries used. It has many drawbacks one major drawback with these batteries are during stand by use. (i.e) In long duration under float charger they develop positive grid corrosion, which will reduce the back up time provided by it.

A good quality of automobile lead acid battery has a life of only about 250-300 full charge / discharge cycle.

Tubular/Industrial lead acid battery

This type of batteries are designed for the heavy duty charge required.

The operating life is more than 1000 charge/discharge cycles. These type of battery requires regular maintenance. Because of the acid in these batteries irritating smell gases and it can not be kept in computer rooms and other AC rooms.

Sealed maintenance free (SMF) batteries

These batteries are completely sealed, so they do not require any kind of regular maintenance. In side of battery, do not contain any wet acid, (ie) lead paste batteries. It is small in size, and it can be kept in the ac room along with inverter.

It is more expensive when compared to the other batteries. It is more sensitive than other batteries. If the operating temperature is more than 40 degree centigrade half the capacity and life of batteries are reduced to half.

Nickel cadmium batteries

These are very expensive batteries and used in defence, space, nuclear science etc applications. It has extra any life operation.

Rating of battery

Commonly the batteries are available in 6V, 12V, 24V, 48V, and 120V and so on. Normally 6, 12 and 24 V rating are mostly available. The capacity of the battery is rated the Ampere/Hour (AH)

The back up time depends on the AH capacity of the battery. Higher the AH capacity more the back up time.

Charging of battery

The life of battery is very much depends on the charging method used to charge the battery.

Three types of charging used to charge the batteries.

- Constant voltage
- Constant current
- Constant voltages- constant current


Constant voltage

This type of charging method using series regulators is suitable for the SMF batteries but not useful in automobile and tubular lead acid batteries.

Constant current

This charging method using shunt regulators, is useful for automobile and tubular /Industrial lead acid batteries, but it can damage the SMF batteries by overcharging them.

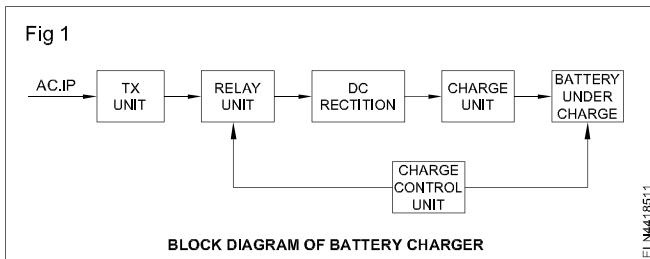A simplified block diagram of battery charger is explained to understand the function of battery charger. (Fig 1)



Transformer

The mains transformer primary is connected through auto transformer and the supply to auto transformer controlled through relays. The automatic charge control supply is always present at the primary of charge control unit transformer.

Relay unit

The relay unit supplies the DC rectifier input supply to the required DC input to the battery for charging. This relay unit also cut-off the rectifier input AC in case of the battery is fully charged.

DC rectifier

This rectifier unit always is a full wave bridge rectifier to handle heavy charging current. High current metal rectifiers are found mostly used in this circuit, but high current capacity semi conductor diode are in use.

Charging unit

This indicates the charging current taken by the battery and it is controlled by ON-OFF switches. A test switch is provided to test the charging condition of the battery.

Battery section

The battery under charger is always to kept in a well ventilated room and also open the vent plug for easy evaporation of exhausted gases from cells.

Charge control unit

Once the battery fully charged; then the DC supply to battery to be cut-off automatically. The voltage sensing circuit enables the control unit to trip the AC input to the rectifier unit thereby stop the charging voltage.

Constant voltage

This type of charging method using series regulators is suitable for the SMF batteries but not useful in automobile and tubular lead acid batteries.

Constant current

This charging method using shunt regulators, is useful for automobile and tubular /Industrial lead acid batteries, but it can damage the SMF batteries by overcharging them.

Constant voltage and constant current

This charging method contains more advantages .This method is suitable for automobile and tubular /Industrial lead acid batteries and also for SMF batteries.

This method provide regulated charging to improve the battery life.

Charging operation of battery

When the mains A.C is available, the mains supply is connected to 0-240V taping of auto transformer through a relay.

The transformer works on step down which has 0-240 V, taping at the primary and 12-0-12 V at the secondary.

The voltage at the secondary is used to charge the batteries connected.

Trickle charging

In an inverter, when the mains A.C is available the battery get charged. After the battery is fully charged the charger is cut-off. After the battery get fully charged if the charger is not cut off then the battery will get damaged.

Trickle charging is a special charging method used to keep the battery constantly in full charge position by keeping the battery charged constantly.

This method of charging is slightly different from the normal charging method.

For trickle charging 100th part of the normal charging current is provided to the battery.


A Simple battery charger

The charger can charge 6V, 12V and 24V battery at Suitable current rate. This circuit has many protection built in it to protect the battery from overcharge and reverse polarity etc.

The charger consist of an auto transformer X₂, (Fig 2) for supplying constant current and voltage.

A charger transformer 'X₁' is connected to the auto transformer and the secondary of the X₁ (Fig 2) is rectified through full wave bridge rectifier and supplied to the battery under charger through. Ammeter voltmeter and a potentiometer (Fig 2)

Fig 2

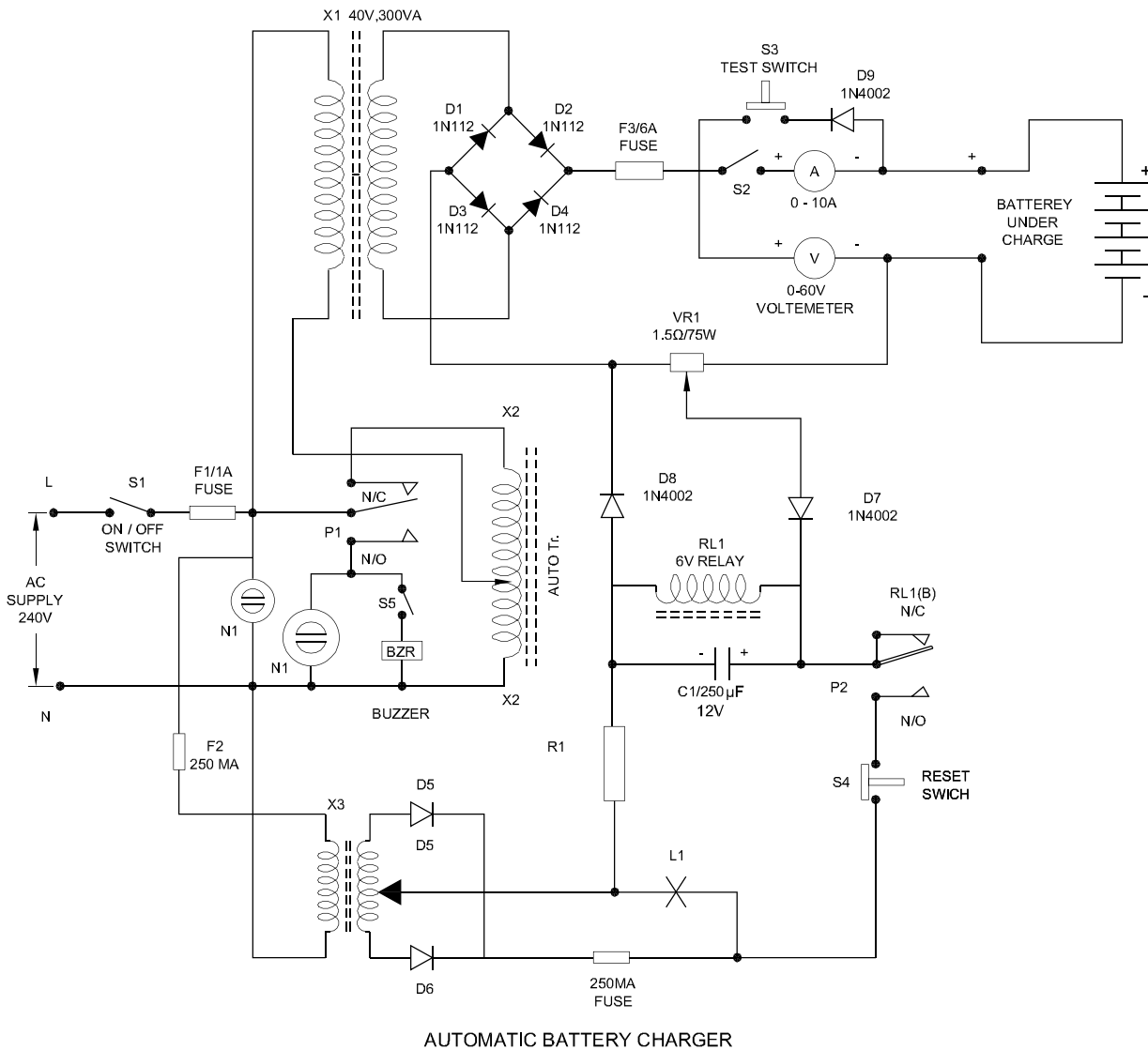

AUTOMATIC BATTERY CHARGER

ELN4418512

A step down transformer X_3 is used to keep cut off relay in energised condition when the mains AC supply is cut off to the charger circuit. Relay RL_1 used to cut off the AC mains supply to the charger circuit. Pole P_1 of relay RL_1 is connected to AC mains supply and pole P_2 is connected to cut off circuit.

Relay is energised by the centre tapping of potentiometer, which is set such that, the current in the charger circuit exceeds then it is energised and poles P_1 & P_2 are connected to normally opened (NO) pin, switching 'Off' A/C mains supply to the circuit.

The test switch S_3 is connected to check battery polarity, reset switch S_4 is used to reset the charger, when any fault occurs. Then the charger is cut off and the Switch ' S_1 ' is mains ON/OFF switch.

A fully charged lead acid battery must be 2.1 volt/cell during on charge. It will increase upto 2.7V/cell. The voltage of a battery is multiple of the number of cells.

In discharged condition the voltage is 1.8V/cell, it should not be further discharged in this condition as it may permanently damage the cell.

E.g A 100AH (ampere hour) battery requires (100 AH/10Hr=10 Amp) 10 Amp. Charging current for 10 hours for fully charged. To get complete discharge at the rate of 5Amps will require 20 Hrs.

The fully discharged battery requires about 1 1/2 times more to get charged. If the battery is in dead (or) not in use for long time even in normal charging current is passed. These dead batteries require higher charge voltage to start the charging current.

Checking of battery

Acid level and specific gravity of electrolyte, will indicate the condition of battery whether it requires charging or not.

The hydro meter is used for checking the acid level in a battery. The scale is marked in the hydrometer from 1100 to 1300. When it is inserted in the battery, the reading

- i) 1100-1150 -indicates battery is down
- ii) 1200-1250- indicates battery is o.k.
- iii) 1250-1300 indicates excess acid

Voltage testing

By using high rate discharge tester, the voltage of each cell must be 2.1V. If it indicates below than 1.8V, then it shows the battery is in fully discharged. It is still below 1.8V. Then the battery becomes dead condition.

Never connect the high rate discharge tester for long duration while checking voltage, it will load the battery heavily and the cell, will discharge.


If the electrolytic level down in the container shell of the battery, top up with distilled water. Never add electrolyte prepared separately to the battery.

In a lead acid battery the electrolyte level of the battery should be checked and maintained every 15 days in summer season.

Inverter

It is an electronic device, which converts a D.C potential (voltages) normally derived from a lead-acid battery into a stepped-up AC potential (voltage) which is similar to the domestic AC voltage.

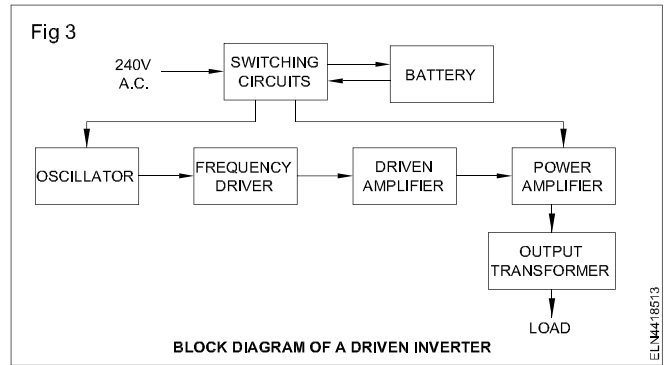Locating the fault and troubleshooting of an inverters which provide sine wave outputs or the use of PWM(Pulse Width Modulation) technology is very difficult. (Fig 3)



Switching circuits


It is the input stage of an inverter. This circuit supplies the power to further stages and is connected to the battery. The DC supply of the battery in this supplies to the switching circuits for various needs.

Oscillator

It is an electronic circuit which generates the oscillating pulses either through an IC circuit or a transistorized circuit. These oscillations are the production of alternate pulse of positive and negative (ground) voltage peaks of a battery and at a specified frequency (No. of positive peaks per second). These are generally in the form of square waves and the inverters are called square wave inverters.

The complete circuit diagram of a static 50Hz static inverter is in Fig 4.

The oscillator section of the inverter uses an IC circuit to produce control signal frequency to the control and driver section. The received oscillating frequency is amplified to a high current level using a power transistor or MOSFET. IC 7473 (JK Flip type) is used for power amplification and control of the frequency to the driver transistors T1 and T2 driving the power transistor to the required level as in Fig 4.

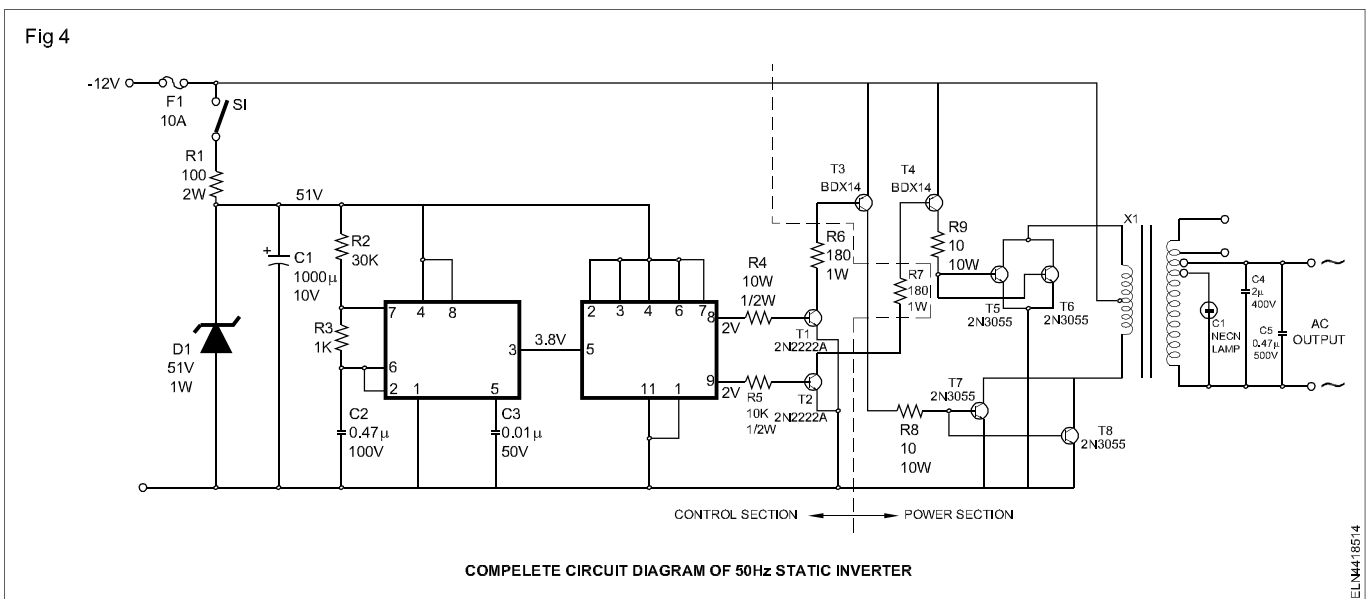

The two parallel connected power transistor T5, T6 and T7, T8 are connected to the output transformer which is used to step up the low level AC from the amplifies stage into the specified level.

The transformer secondary is supplied the required level of AC 240V. The generation of the oscillations due to which the process of voltage induction is able to take place across the windings of the transformer.

The inverter does not produce any power and the power produced by DC source. The inverter requires a relatively

stable power source capable of supplying of enough current for the intended power demands of the system.

An inverter can produce square wave, modified sine wave, pulsed sine wave, pulse width modulated wave (PWM) or sine wave depending on circuit design.

The inverters more than three stages are more complex and expensive. Most of the electric devices are working with pure sine wave and AC motors directly operated on non-sinusoidal power may produce extra heat, and have different speed-torque characteristics.

Stabiliser, battery charger, emergency light, inverter and UPS

Objectives: At the end of this lesson you shall be able to

- state the general precaution to carryout for preventive maintenance
- explain the steps to follow the break down maintenance
- service the voltage stabilizer, emergency light, battery charger, inverter and UPS
- analyse the trouble shooting chart and find the problem/ repair the equipment.

Use of flow chart and troubleshooting charts for fault location :

The circuit diagram in Fig 1 is given for your reference. The working of the mains cord, fuse, relay contacts, windings of the auto-transformer etc. can easily be ascertained by using a test lamp and/or a series lamp or by a voltmeter for checking the electronic circuit and relay coil winding. A multimeter in appropriate range is a must to localise the fault. A series lamp or test lamp should not be used to test these as they are liable to spoil while testing.

Method of trouble shooting : Referring to Fig 1, we find that the absence of control voltage from S₁, S₂ or DC voltages will make both the relays inoperative, and, hence, will be in the off position resulting in higher output voltage than input voltage with boost indication. The same result also occurs when both transistors are open.


When both the transistors are short i.e. collector to emitter is short or both zener diodes are short the relays are energised and the output voltage will be lower than input voltage.

When one of the relay circuit is only not operating that particular function will be absent i.e. either back or boost function will be absent.

When a component mounted on PCB is suspected to be defective, first ascertain from all possible tests with in the circuit and then remove the component from PCB only when it is absolutely necessary. Even removing components for testing should be done as rarely as possible.

While removing the components from PCB, the component position with respect to the PCB, the terminal connections and hook up wire connections should be noted to enable the electrician to reconnect the component properly. When replacing the components procure the component of the same specification or equivalent so that the performance of the equipment is not affected after repair.

Troubleshooting chart given in Table 1 illustrates the problem, section to be suspected possible cause and action required for a stepped automatic voltage stabilizer.

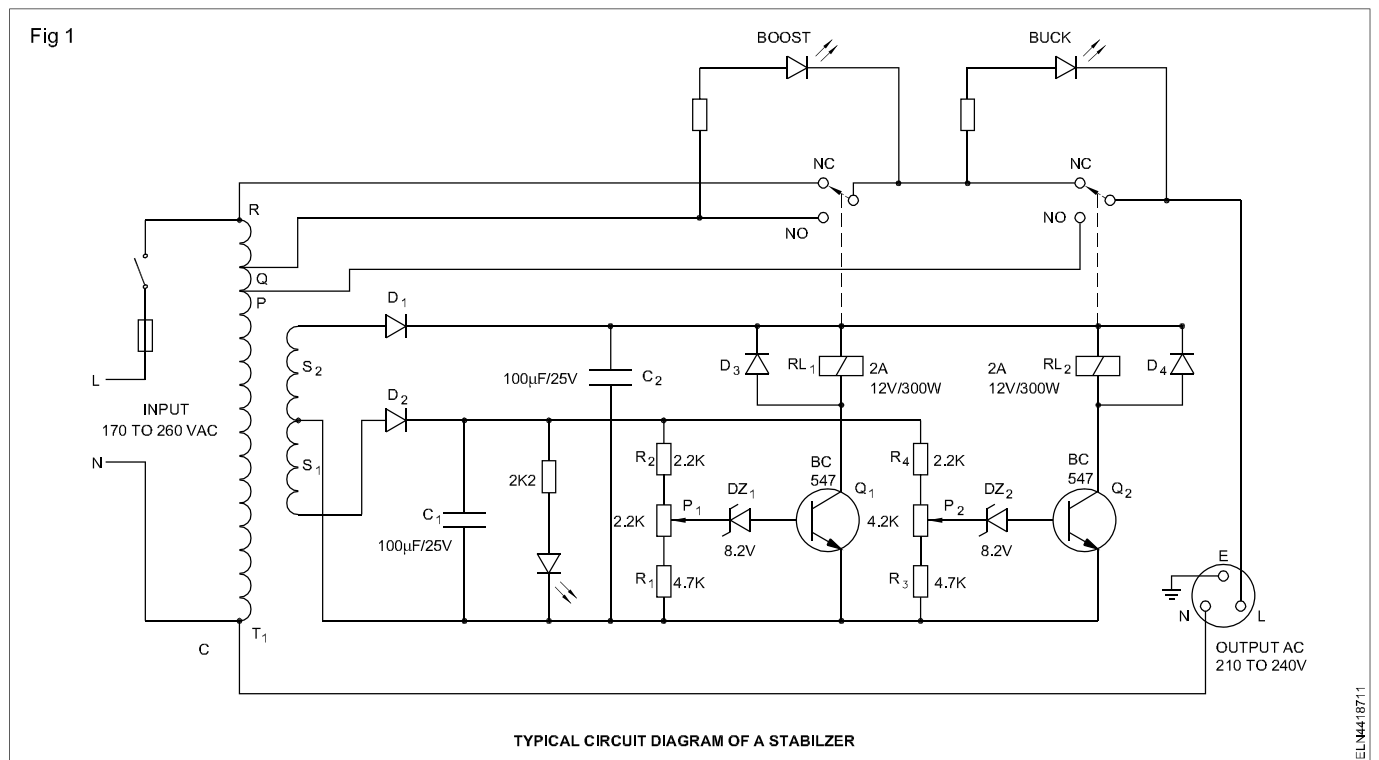

ELN4418711

General precautions for preventive maintenance

Maintenance for any equipment needs a working knowledge of that machine is very much essential to the person concerned. For example the volt ampere rating of voltage stabilizer is very important to carry out the preventive maintenance. Low quality, substandard components or materials never be used or recommended for use. Necessary steps to be taken for safe temperature controlling and over loading conditions. Proper operating sequence or working steps to follow of all the equipments under maintenance.

Steps to follow break down maintenance

Break down can happen anytime, anywhere. Adequate protection might have provided to all equipments, for its smooth working. However continuous running or usage,

lack of maintenance, human error and some unexpected reasons break down is happening.

Once break down maintenance or repair is required a detailed study of that equipment is essential. Always involve more persons pertain to the repair work or maintenance work for achieving a good result. A collective and competitive effort only will produce good results. Give value for everyones suggestion, expertise and workmanship. There must be a clear idea and vision to finalise the maintenance and repair. Ensure the services of experts, availability of spares, details of past records, diagrams and past history of the equipment such as its installation date, service records, number of break downs and its frequency etc; Servicing of voltage stabilizer by trouble shooting method.

Table 1

Trouble shooting chart for stepped automatic stabilizer

Sl. No.	Problem	Section to be suspected	Possible cause for defective	Action
1	No output voltage at output socket.	Input buck/boost relays.	Mains cord, switch, fuse, transformer and relays	Locate and repair or replace
2	The output voltage is more, do not regulate.	Electronic circuit or relays.	Open/shorted rectifier / diodes, or open zener diodes	Locate the defective part and replace.
3	Output voltage is same as input. Do not regulate.	Transformer or Electronic circuit	Transistor or held up relay contacts or Partial open transformer / leads.	Test, repair or replace.
4	Output voltage is low. Do not regulate.	Electronic circuit	Shorted zener diode or transistor or open resistors	Test and replace.
5	Chattering in relays	Electronic circuit/relays	Leakage capacitors	Replace.

Trouble shooting of UPS

The trouble shooting and repair of UPS is difficult as this circuit is so complicated with so many functions. A step by step trouble shooting approach with a reasonable analysing

is very important to carry out the troubleshooting in the UPS circuit.

A trouble shooting chart of UPS is given for your reference in table - 2.

Table 2

Troubleshooting chart of UPS

Sl.No.	Fault	Possible Reason	Troubleshooting
1	UPS works on 240V VAC mains but does not operate on battery	1 Battery fuse is blown out 2 Battery is discharged	1 Check the battery fuse. If fuse is blown, replace it, if it is loose, tighten 2 Recharge the battery, also check the polarity of battery
2	When UPS is switched on, charger does not turn on	1 Mains input fuse may be blown	1 Change mains fuse, if fuse blown

SI.No.	Fault	Possible reason	Troubleshooting
		2 Charger input fuse blown out	2 Check the battery polarity and conditions, correct it if wrong, replace the fuse 3 Check the supply from mains, if OK, then check relay wiring, check relay coil.
3	240 VAC mains supply NOT available	1 Mains supply fails 2 Input AC mains is very low 3 Loose connection in input wiring	1 Check the supply of mains 2 Check the voltage 3 Tight the connection of wiring coming from distribution board
4	DC voltage is OK, but UPS shows DC under voltage and trips	1 Inverter fuse is blown 2 Rust/loose connection in battery	1 Replace fuse 2 Check the connection
5	When the UPS is switched ON with out load but DC under voltage indicator turns ON at load.	1 Load too high 2 Loose connection of battery terminal 3 Short or earth fault in load	1 Check the load, add loads gradually. 2 Tight the connections and check the polarity of battery 3 Check the load circuit wiring
6	Where there is no AC mains supply and the UPS is operating on battery, DC under voltage indicator turns ON	1 Battery is discharged 2 Battery terminal dust or loose	1 Recharge the battery, use proper current capacity cable in the battery circuit. 2 Check the connection
7	DC fuse blows OFF	1 Overload or short circuit	1 Change DC fuse 2 Reduce the overload. If power transistors are short or leaky, replace them.
8	UPS does not switch ON	1 Supply fails due to blown out fuse or some break in cable 2 No DC supply in the control card due to dry soldering or desoldering	1 Replace fuse, check the cables 2 Check and correct dry soldering and de-soldering 3 Check control card wiring
9	UPS trips when full load is connected	1 Overload setting is wrong	1 Adjust the overload setting, check the power consumption of the load. Gradually increase the load.
10	UPS output is high	1 Some connection is broken in the feedback loop 2 Control card is not functioning properly 3 Over voltage sensing is faulty	1 Check feedback transformer wiring and adjust feedback voltage preset. 2 Check /Replace control card 3 Check overload sensing circuit
11	UPS does not switch on in battery mode	1 Mains earthing is not proper 2 Problem in inverter circuit	1 Check the earth connection 2 Check battery, MOSFET, oscillator section, driver section, output section
12	Battery wire getting burned	1 The relay points are joined together	1 Check / Replace relays

SI.No.	Fault	Possible reason	Troubleshooting
13	Change over time high, computer connected to the UPS reboots during change over.	1 Check oscillator circuit	1 Check /replace IC and other components of oscillator section
14	Low backup time	1 Main filter capacitor problem 2 Battery get short circuit/discharge	1 Check and replace capacitor 2 Check battery, replace if required

Trouble shooting of battery charger and emergency light

As you have seen that the battery charger is a simple circuit compare to UPS. The main function of the charger circuit is to feed the DC voltage to battery at a prescribed

level we discuss only the trouble shooting of charger circuit and its repair. Battery maintenance is not discussed in the trouble shooting chart.

Analyse the fault in battery charging circuit (Fig 1) with the help of trouble shooting chart given in Table 3 and 4.

Table 3

SI. No.	Problems	Section to be suspected	Possible cause for defects	Action
1	No DC voltage at charging terminal	1 Faulty Ammeter (open circuit) 2 Blown fuse 3 Faulty rectifies diode 4 Defective transformer 5 Faulty Relay contacts 6 Open Relay coil 7 Main fuse blown 8 No link between meter to battery 9 Defective auto transformer	Aged/over current Over current Aging/over loading Aging/over loading Repeated closed open Over voltage/current Over loading Loose connection Over loading	Replaced Ammeter Replace fuse Replace all diodes Replace transformer Replace contact Replace relay Replace fuse Tighten the connection Replace transformer
2	Low terminal voltage	Anyone pain diode open circuited Partial short in transformer	Ageing Over heat	Replace all four diodes Replace transformer
3	No automatic charging voltage cut off	Defective potentiometer Driver diode open Defective electrolytic capacitor Defective bleeder resistor Control circuit rectifier diode open LT winding transformer open LT fuse open Defective auxiliary relay terminal	Long use Ageing Ageing Over current Ageing Over current Ageing / over current Over current Repeated operation	Replace new potentiometer Replaced 2 diodes(D7) Replace capacitor (C ₁) Replaced same value resistor(R ₁) Replace both diodes(D ₅ & D ₆) Replace new transformer (x ₃) Replace fuses (F ₂) Replace contact RLI(B)

Table 3 contd...

SI. No.	Problems	Section to be suspected	Possible cause for defective	Action
4	Irregular over voltage cut off	Defective potentiometer Shorted driver diode Loose in relay contacts leaky electrolytic capacitor	Loose contact in the disc (track) ageing/over current Repeated contacts ageing	replace new potentiometer (VP1) replace new diode (d7) replace contacts replace electrolytic capacitor

Table 4

Trouble shooting chart for emergency light

SI No	Problems	Section to be suspected	Possible cause for defective	Action
1	Lamp dead in both condition lamp	Defective tube Defective inverter transformer Defective driver	Ageing Over loading/ageing Over loading/ageing transistor	Replace tube lamp Replace inverter transformer Replace transistor (213055)
2	Lamp out glowing if AC fails	Low/ dead battery	Ageing	Replace New battery

Servicing of equipment are discussed based on a sample circuits. When servicing of other equipments with different circuits may differ from the troubleshooting sequences. However the basic principle based on the block diagram may be taken for guidance to service/repair the equipment.

Trouble shooting of inverter

DC to AC inverter is quite complicated circuit, it consists of many functions. The switching circuit, oscillator circuit, control circuit power amplifier circuit, driver, finally the output circuit through the transformer. A feed back is also

taken from the output transformer to regulate the output through the control circuits.

A constant DC source; either from a converter or battery is very much essential to keep the power output in a constant stage. DC to AC conversion with a specified frequency and a particular wave is difficult.

Analyse the fault in a inverter is explained (Fig 2) with the help of trouble shooting chart is given in Table 5. However the fault and problem are discussed while considering the 50Hz static inverter circuit is in Fig 2.

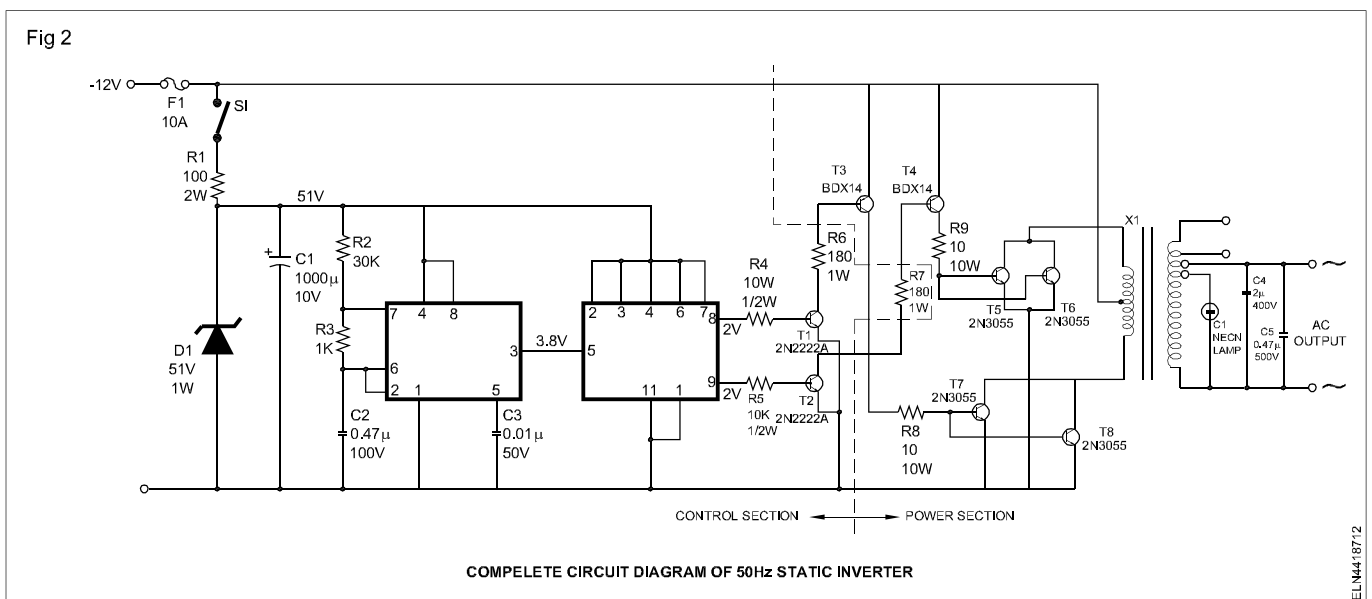


Table 5

SI No	Problems	Section to be suspected	Possible cause for defects	Action
1	Output - Dead	- Output transformer - DC source	- Transformer open or short - CT & transformer open - No DC from battery - Battery dead	Rectify transformer Rectify the CT connection Replace battery
2	Low or high frequency	- Oscillator IC (555) - Control IC JK Flip-Flop	- Faulty IC - Faulty IC - No supply to IC (series resistor open) - Capacitor connected to IC 555 shorted	Replace IC Replace IC Replace resistor Charge faulty capacitor
3	Low voltage frequency ok	- Driver transistor - Power transistor (output transistor)	Fault in driver transistor Fault in power transistor Fault in output transformer Partial short in winding / cave	Charge the transistor Replace the power transistor Rectify the transformer fault or Replace the transformer
4	Frequent cut-off the output	- Battery - Fault in IC - Fault in power transistor	- Low A/H capacitor of battery - Over heat in IC - Over heat in power transistor	Replace Battery Provide heat Sink to IC Sink to transistor

Installation of inverter in domestic wiring

Objectives: At the end of this lesson you shall be able to

- enumerate the important points to be kept in your mind to select the inverter to be installed
- state how to select the place to install the inverter and battery
- explain how to install the inverter with battery and load, and check for its performance
- state the rating of inverter and its sample calculation.

Important points to be considered before installing an inverter

Many time when a new inverter is not giving proper service, the fault is due to improper installation only, not in inverter.

Another most important point is when connecting an inverter to the line is, the total load connected to the inverter should not exceed 80% of capacity of inverter.

Before providing points to connect the loads to the inverter, the total connected load must be considered.

If over load occur, then the overload protection will 'cut OFF' the output and reduce the load then the reset key must be pressed, and if the inverter is not provided with overload protection, it may get damaged at the time of over load than the capacity of the inverter.


Selection of place for installation of inverter

To connect inverter to the supply line, suitable place for the inverter is to be located. That place must be nearer to the service energy meter and ICDP switch and provide a 3 pin output socket from the mains supply line for the inverter and connect the inverter to the socket as in (Fig 1).

Installation of inverter

Collect the suitable inverter with sealed free maintenance battery to be installed, and check for their proper function

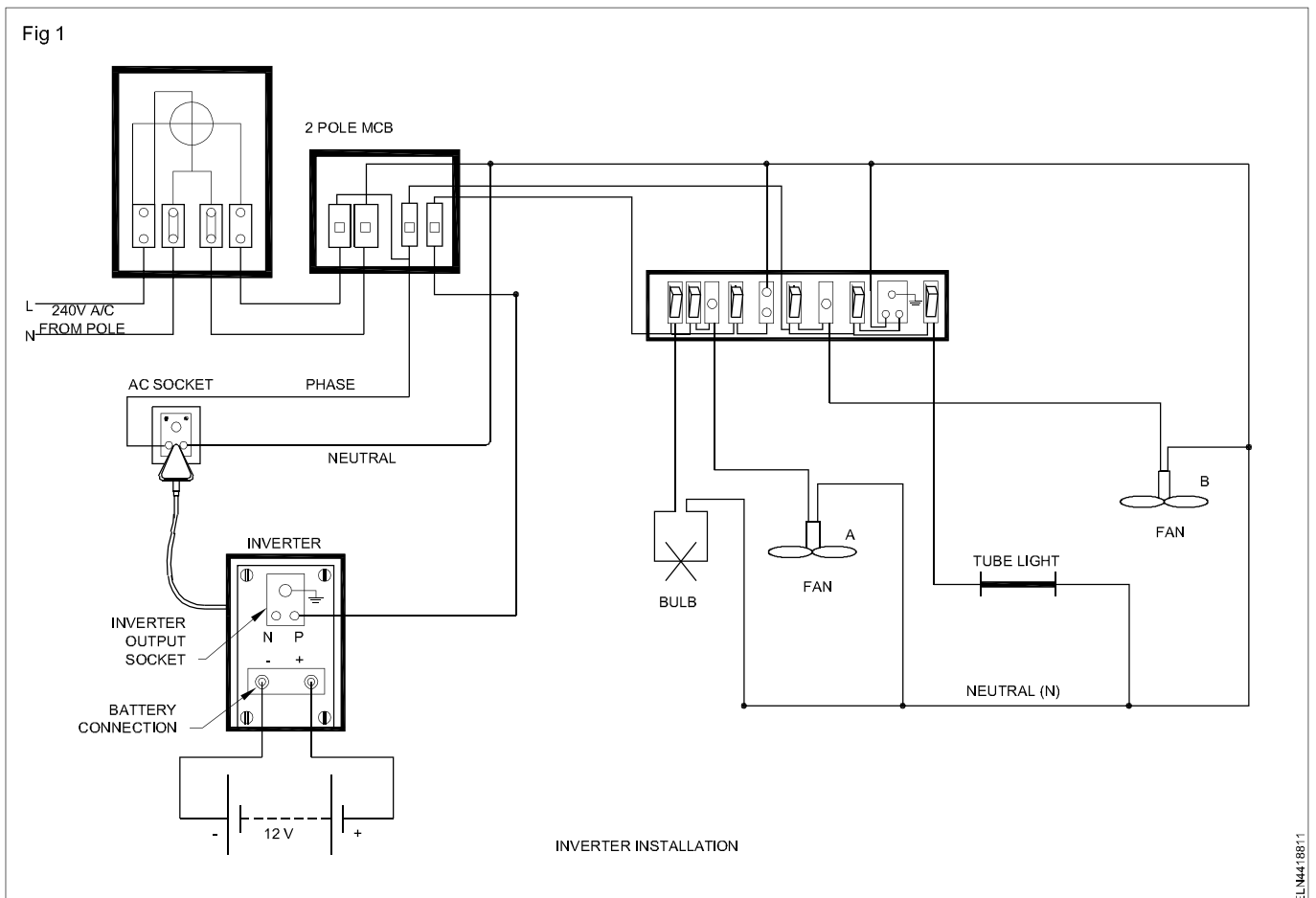Place the inverter's battery to a suitable place near the inverter and connect the battery to the inverter.(Fig 1)



Keep the battery as close as possible to the inverter, so that the wire connecting the battery terminals to the inverter can be small and current loss is reduced. Make sure the battery is fully charged before installation.

The positive terminals of battery (red wire) is connected to the place provided for the positive terminal on the inverter and the negative terminal of the battery (blue or black wire), which is to be connected to the place provided for the negative terminal on the inverter.

When connecting battery terminals to the inverter, use special auto wires do not use common mains wiring with wires such as '3/20' and 7/20 etc. connecting battery using these wires will not provide proper connection between the battery and the inverter.

After connecting the battery, put some grease (or) vase-line on the battery terminals, which reducing the terminal corrosion.

All the connection is completed take the output from the inverters output socket and use it to power the load. Use 1/18 copper wire to the output of the load. Do not use 3/20, 3/22 or 7/20 wires, commonly used in house wiring.

The output is taken from the phase out 'pin of inverter' output socket, and is provided to the ON/OFF switches on the wall pause.(Fig 1)

The neutral line is common for both the inverter output and the mains A/C line. So, only one wire for the phase

line can be drawn from the inverter output socket to the switches.

In Fig 1, one bulb, one fan and a 2 pin output socket are connected to the inverter output and the other devices in the room. (ie) the tube light, fan (2) and a 3 pin output socket are directly connected to the mains A/C line.

In the two pin socket, should not be connected with heavy load during power 'OFF' only small load like mosquito repeller can be connected.


As in (Fig 1) the load connected to the inverter will get the mains A.C supply. If the mains supply is 'On' at the same time, other devices will also work on the main supply, because they are connected directly to the mains A.C supply.

But at the time of power shut down, the devices directly are connected to the mains A.C will stop functioning and the devices, which are connected to the inverter output will keep on working on the inverter output.

Later, if the mains A.C supply returns, the inverter will once again connect the load, which are connected to its output to the main supply. This process is in Fig 2.

Inverter rating calculation

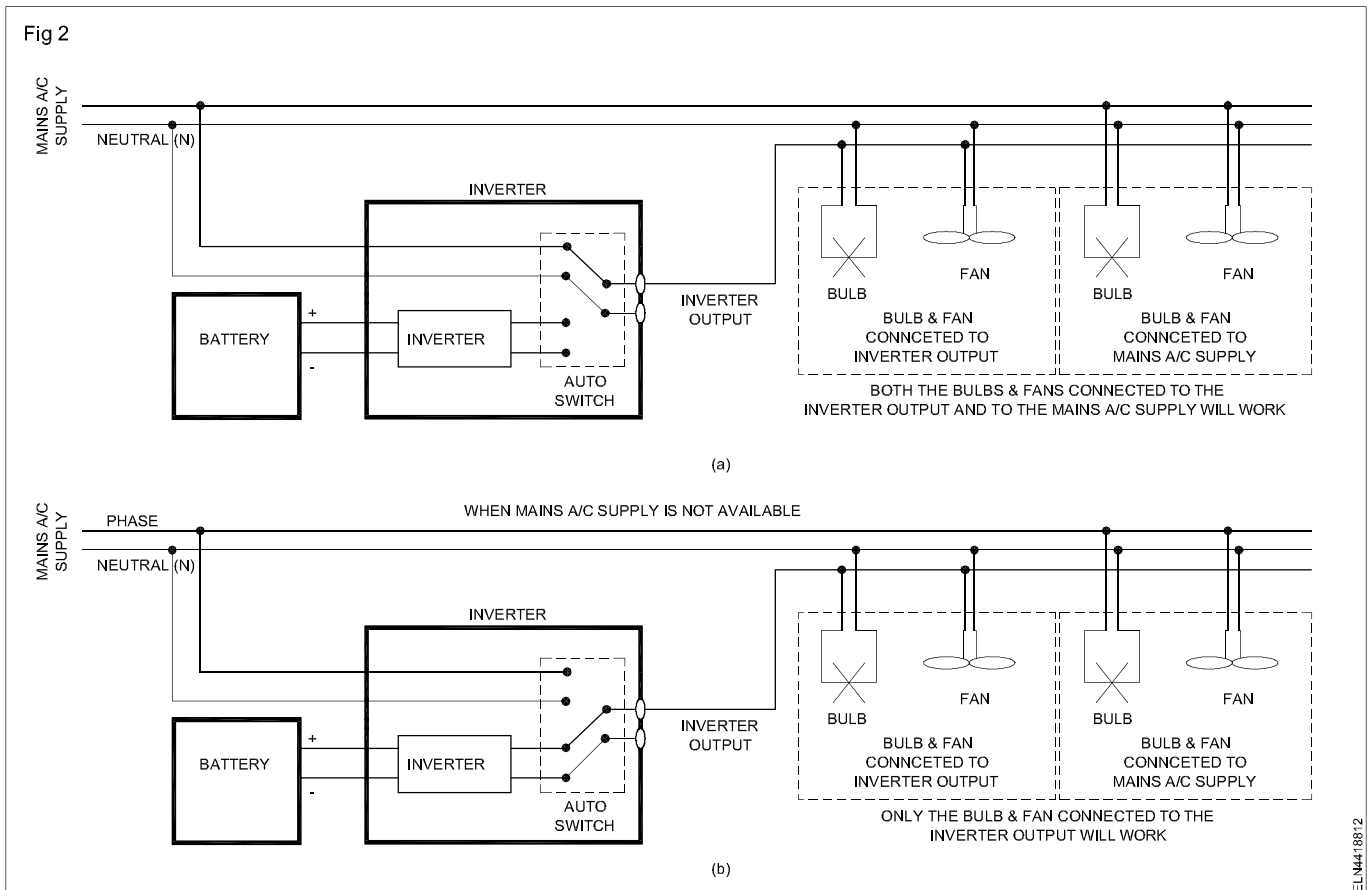Generally, the inverters are available with ratings such as 200w,300w,400w,500w,600w,1000w,1200w,1500w and so on.



The cost of the inverter is proportional to their capacity in wattage (or) VA. It must be considered before buying the Inverter.

Calculation of power consumption

True power = Apparent power x power factor

Let us assume,

The loads are - 2 tube lights, (ie) $2 \times 40W = 80W$
 - 1 fan (ie) $1 \times 60W = 60W$
 - 1 bulb (ie) $1 \times 40W = 40W$
 Total load = 180 W

If the total load is 180W, the inverter capacity is to be selected for 300W, giving some safe margin.

Always, the inverter with high rating must be purchased by considering the future the household appliances may be added.

Power consumption Table

Device time	Approx Watts	P.f-0.8 (app) VA	Running for 1 unit of consumption (approx.) Hrs. - Min.
Incandecent bulbs (B.C bulbs)	25W	20	40-00
Incandecent bulbs	40W	32	25-00
Incandecent bulbs	60W	48	16-40
Incandecent bulbs	100W	80	10-00
Fluorescent tube 61 cms	20W	16	50-00
Fluorescent tube 122 cms	40W	32	25-00
4 feet night lamp	15W	12	66-40
Mosquito repellent	5W	4	200-00
Fans	60W	48	16-40
Air - coolers	170W	136	5-50
Air-conditioners (1 to 1.5 ton)	1500W	1200	0-40
Refrigerators (165 liters)	225W	180	4-30
Mixer/blender /juicer	450W	360	2-15
Toaster	800W	640	1-15

Device time	Approx Watts	P.f-0.8 (app) VA	Running for 1 unit of consumption (approx.) Hrs. - Min.
Hot plate	1000W	800	1-00
Oven	1000W	800	1-00
Electric kettle	1000W	800	1-00
Iron	450W	360	2-15
Water heater: (a) Instant geysers 1.5 - 2 liter)	3000W	2400	0-20
Water heater: (b) Storage type (10-12 liter)	2000W	1600	0-30
Water heater: (c) Immersion rod	1000W	800	1-00
Vacuum cleaner	700W	560	1-25
Washing machine	325W	260	3-00
Water pump	750W	600	1-20
TV	60W	48	16-00
Radio	15W	12	66-00
Video	40W	32	25-00
Tape recorder	20W	16	50-00
Stereo system	50W	40	20-00
PC Cop.	120W	150	8-20
PC/XT cop.	185W	230	5-25
PC/AT Cop.	255W	320	3-55
386& Higher Cop.	320W	400	3-08
Mono chrome monitor	44W	55	22-45
CGA monitor	64W	88	15-35
EGA monitor	80W	100	12-30
VGA monitor	120W	150	8-20
80-column dot-matrix printer	64W	80	15-40
160-240 cps printer	100W	125	10-00
132- column dot matrix printer	140W	175	7-08

Device time	Approx Watts	P.f-0.8 (app) VA	Running for 1 unit of consumption (approx.) Hrs. - Min.
Image writer II	80W	80	12-30
Laser write plus	880W	1100	1-08
HP Laser jet Printer	840W	1050	1-11
External Hard Disks	80W	100	12-30
Tape Back up	140W	175	7-08

Preventive and breakdown maintenance

Preventive maintenance : It improves the performance safety of a business instead of a large repairs being needed and major problems arising. Consistent maintenance is carried out to reduce these risks. This improves the performance of all equipment. It also helps to avoid unplanned repairs and unexpected maintenance needs.

Preventive maintenance further divided into two parts they are;

- a Planned preventive maintenance and
- b Unplanned preventive maintenance

a Planned preventive maintenance

A planned preventive maintenance cut-down maintenance cost and ensure the long life of equipment and a steady quality output. The following is the benefits of planned preventive maintenance.

- a overtime costs reduced
- b reduced risk of problems
- c reduced no. of repairs
- d small repairs can be carried out regularly

- e ensures all equipment safe in good conditions
- f If meets safety and environment standards
- g Improves the safety and health of workers.
- b Unplanned preventive maintenance

The unplanned preventive maintenance is nothing but a routine maintenance work. For example lubricating, cleaning, tightening of nuts and bolts etc, are same of the maintenance. This not involves any predetermined work associated. The following is the draw backs of unplanned preventive maintenance.

- a Increases overall material cost
- b Improper usage of manpower
- c Not guaranteed of quality or quantity in production
- d No guarantee of machine condition
- e Increased risk of problems
- f Unexpected problems in production and quality.

Breakdown maintenance is a form of material or equipment remediation that is performed after the equipment or material has lost its functioning capabilities or properties.

Breakdown maintenance is maintenance performed an equipment that has broken down and is unusable. It is based on a breakdown maintenance trigger.

Demerits of breakdown maintenance

- a Loss of production and business unexpected
- b Huge expenses for restoration
- c Non availability of spares and experts
- d Accidents, environmental problems
- e Leads to major accidents loss of life
- f Wastage of raw material if time based supply

A well planned preventive maintenance can avoid breakdown of machines and keep maintain steady quality production and maintain company standards.